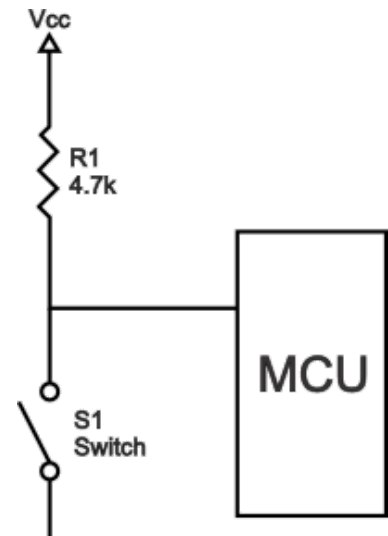


PULL UP RESISTOR / PULL DOWN RESISTOR

- What are pull-up resistors?
- Pull-up resistor definition
- What are pull-down resistors?
- Pull-up resistor value
- Typical applications for pull-up and pull-down resistors

What are pull-up resistors?

Pull-up resistors are resistors used in logic circuits to ensure a well-defined logical level at a pin under all conditions. As a reminder, digital logic circuits have three logic states: high, low and floating (or high impedance). The high-impedance state occurs when the pin is not pulled to a high or low logic level, but is left “floating” instead. A good illustration of this is an unconnected input pin of a microcontroller. It is neither in a high or low logic state, and a microcontroller might unpredictably interpret the input value as either a logical high or logical low. Pull-up resistors are used to solve the dilemma for the microcontroller by pulling the value to a logical high state, as seen in the figure. If there weren't for the pull-up resistor, the MCU's input would be floating when the switch is open and brought down only when the switch is closed.



Pull-up resistor circuit

Pull-up resistors are not a special kind of resistors; they are simple fixed-value resistors connected between the voltage supply (usually +5V) and the appropriate pin, which results in defining the input or output voltage in the absence of a driving signal. A typical pull-up resistor value is 4.7kΩ, but can vary depending on the application, as will be discussed later in this article.

Pull-up resistor definition

“ Pull-up resistors are resistors which are used to ensure that a wire is pulled to a high logical level in the absence of an input signal.


What are pull-down resistors?

Pull-down resistors work in the same manner as pull-up resistors, except that they pull the pin to a logical low value. They are connected between ground and the appropriate pin on a device. An example of a pull-down resistor in a digital circuit can be seen in the figure. A pushbutton switch is connected between the supply voltage and a microcontroller pin. In such a circuit, when the switch is closed, the micro-controller input is at a logical high value, but when the switch is open, the pull-down resistor pulls the input voltage down to ground (logical zero value), preventing an undefined state at the input. The pull-down resistor must have a larger resistance than the impedance of the logic circuit, or else it might be able to pull the

voltage down by too much and the input voltage at the pin would remain at a constant logical low value – regardless of the switch position.

Pull-up resistor value

The appropriate value for the pull-up resistor is limited by two factors. The first factor is power dissipation. If the resistance value is too low, a high current will flow through the pull-up resistor, heating the device and using up an unnecessary amount of power when the switch is closed. This condition is called a strong pull-up and is avoided when low power consumption is a requirement. The second factor is the pin voltage when the switch is open. If the pull-up resistance value is too high, combined with a large leakage current of the input pin, the input voltage can become insufficient when the switch is open. This condition is called having a weak pull-up. The actual value of the pull-up's resistance depends on the impedance of the input pin, which is closely related to the pin's leakage current.

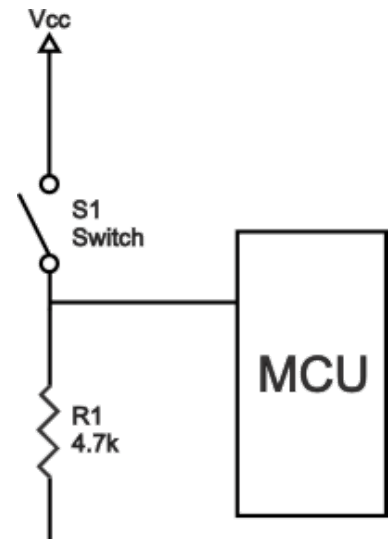

Pull-down resistor

A rule of thumb is to use a resistor that is at least 10 times smaller than the value of the input pin impedance. In bipolar logic families which operate at operating at 5V, the typical pull-up resistor value is 1-5 k Ω . For switch and resistive sensor applications, the typical pull-up resistor value is 1-10 k Ω . If in doubt, a good starting point when using a switch is 4.7 k Ω . Some digital circuits, such as CMOS families, have a small input leakage current, allowing much higher resistance values, from around 10k Ω up to 1M Ω . The disadvantage when using a larger resistance value is that the input pin responses to voltage changes slower. This is the result of the coupling between the pull-up resistor and the line capacitance of the wire which forms an RC circuit. The larger the product of R and C, the more time is needed for the capacitance to charge and discharge, and consequently the slower the circuit. In high-speed circuits, a large pull-up resistor can sometimes limit the speed at which the pin can reliably change state.

Typical applications for pull-up and pull-down resistors

Pull-up and pull-down resistors are often used when interfacing a switch or some other input with a microcontroller or other digital gates. Most microcontrollers have in-built programmable pull up/down resistors so fewer external components are needed. It is possible to interface a switch with such microcontrollers directly. Pull-up resistors are in general used more often than pull-down resistors, although some microcontroller families have both pull-up and pull-downs available.

They are often used in analog to digital converters to provide a controlled current flow into a resistive sensor.

Another application is the I2C protocol bus, where pull-up resistors are used to enable a single pin to act as an input or an output. When not connected to a bus, the pin floats in a high-impedance state.

Pull-down resistors are also used on outputs to provide a known output impedance.

SHARE    

Tags

applications, arduino pull up resistor, i2c pull up resistor, internal pull up resistor, pull down, pull down resistor, pull up, pull up pull down resistor, pull up resistor, pull up resistor calculation, pull up resistor value, resistor, resistor applications, usb pull up resistor, weak pull up resistor

[FACEBOOK](#)[YOUTUBE](#)

@2019 EETech Media, LLC. All rights reserved.

[BACK TO TOP](#)